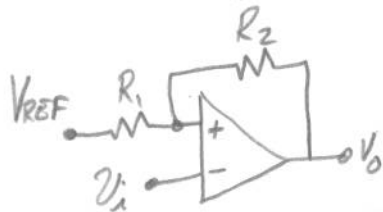


Schmitt Trigger Problem

Pertinent Equations


clamping: $V_S = \left(\frac{R_2}{R_1 + R_2} \right) V_{REF}$



$V_T = V_S + \left(\frac{R_1}{R_1 + R_2} \right) V_O$ ← This is the transition voltage


$V_{T(L \rightarrow H)}$ when V_O is @ negative rail
 $V_{T(H \rightarrow L)}$ when V_O is @ positive rail

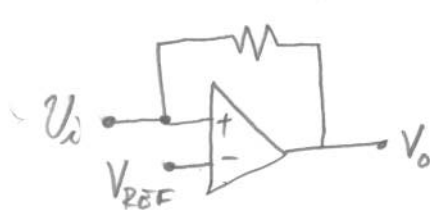Non-clamping: $V_S = \left(1 + \frac{R_1}{R_2} \right) V_{REF}$



$V_T = V_S - \left(\frac{R_1}{R_2} \right) V_O$

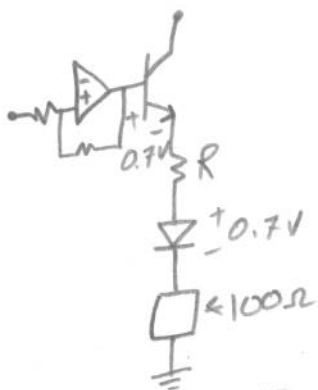Ex 15.7 clamping with $V_S = 1V$; hysteresis width is $100mV$
 $\pm 10V$ rails, $I_R = 200\mu A$ w/ $V_O = +10V$



$1 = \left(\frac{R_2}{R_1 + R_2} \right) V_{REF}$

$V_{T(L \rightarrow H)} = 1 - \left(\frac{R_1}{R_1 + R_2} \right) (10)$ } $V_{T(L \rightarrow H)} = 0.95V$

$V_{T(H \rightarrow L)} = 1 + \left(\frac{R_1}{R_1 + R_2} \right) (10)$ } $V_{T(H \rightarrow L)} = 1.05V$

$\frac{R_1}{R_1 + R_2} = 0.005 \Rightarrow \frac{R_1 + R_2}{R_1} = 200 \Rightarrow 1 + \frac{R_2}{R_1} = 200$


$\therefore \frac{R_2}{R_1} = 199 \quad \& \quad \frac{R_1}{R_2} = 5.025 \times 10^{-3}$

$\left(\frac{R_2}{R_1 + R_2} \right) V_{REF} = 1 \Rightarrow V_{REF} = 1 \left(\frac{R_1 + R_2}{R_2} \right) = 1 \left(1 + \frac{R_1}{R_2} \right)$
 $= 1(1 + 5.025 \times 10^{-3})$

$V_{REF} = \underline{\underline{1.005V}}$

$R = \frac{10 - 1.4 - 100(200\mu A)}{200\mu A}$

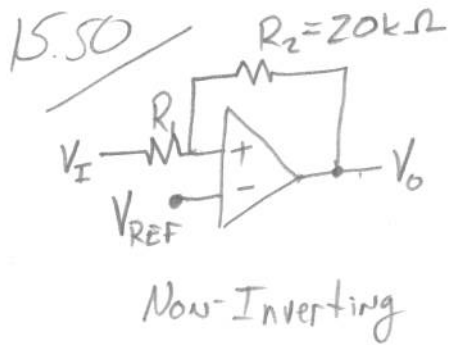$R = \underline{\underline{42.9k\Omega}}$



$$V_S = V_{REF} \left(1 + \frac{R_1}{R_2} \right)$$

$$V_T = V_S - \left(\frac{R_1}{R_2} \right) V_O$$

Rail Voltages: $\pm 12V$

$$\left. \begin{array}{l} V_{T(H \rightarrow L)} = -2V \\ V_{T(L \rightarrow H)} = -1V \end{array} \right\} V_S = \underline{-1.5V}$$

$$-1.5 = V_{REF} \left(1 + \frac{R_1}{R_2} \right)$$

$$V_{T(H \rightarrow L)} = -2 = -1.5 - \left(\frac{R_1}{R_2} \right) 12$$

$$0.5 = \frac{R_1}{R_2} \cdot 12$$

$$\frac{R_1}{R_2} = 0.0417 \Rightarrow R_1 = \underline{\underline{833\Omega}}$$

$$V_{REF} = \frac{-1.5}{1.0417} \quad \text{for } R_2 = \underline{\underline{20k\Omega}}$$

$$\underline{\underline{V_{REF} = -1.44V}}$$

