

Latches and Flip-Flops

ELEC 311


Digital Logic and Circuits

Dr. Ron Hayne


Images Courtesy of Cengage Learning




Set-Reset Latch

 


Set-Reset Latch

 



Set-Reset Latch

 


Set-Reset Latch

 


Switch Debouncing

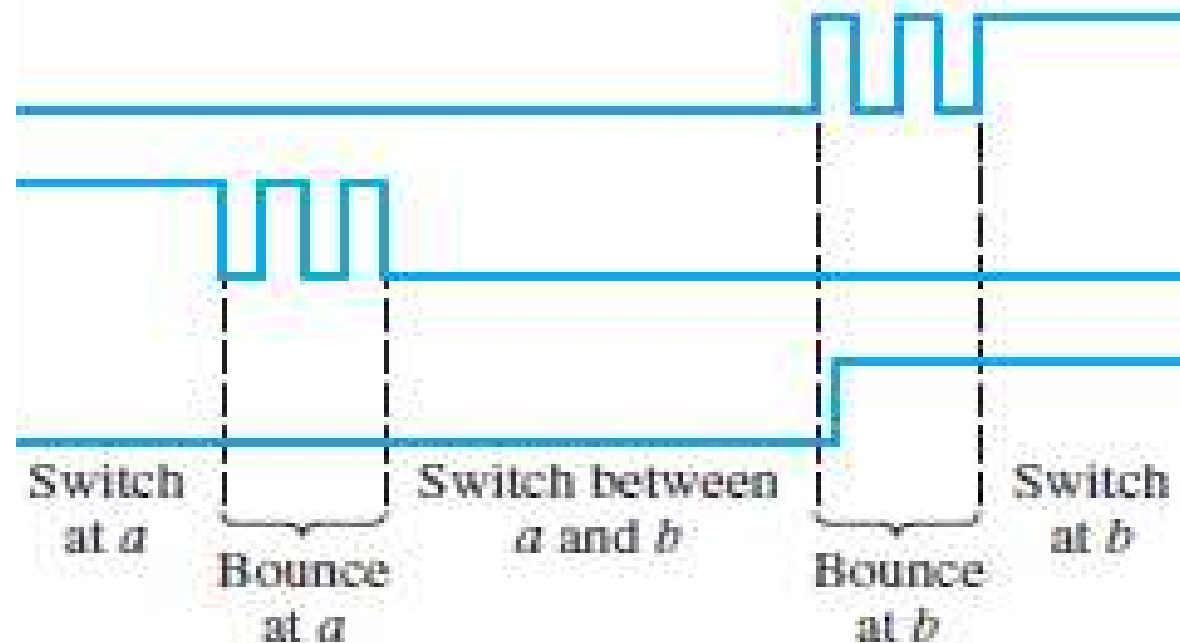 

D Latch

 


Edge-Triggered D Flip-Flop

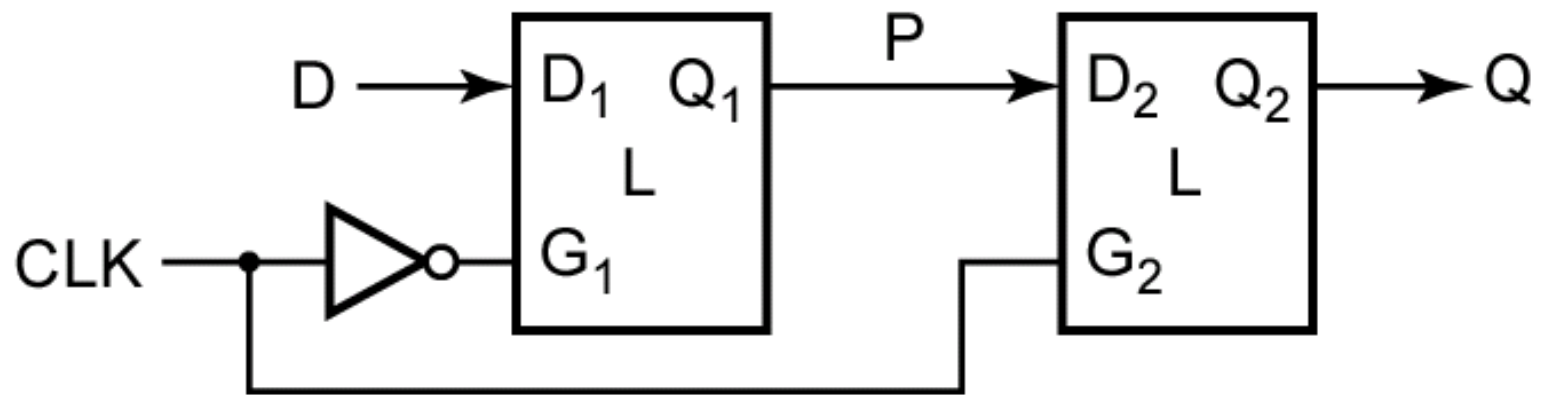



Timing Parameters

FIGURE 11-20
Setup and Hold
Times for an
Edge-Triggered D
Flip-Flop

© Cengage Learning 2014

 


J-K and T Flip-Flops

  

J-K FF Timing Diagram

FIGURE 11-24
J-K Flip-Flop
(Q Changes on
the Rising
Edge)

© Cengage Learning 2014

 


(a) J-K flip-flop

J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^+ = JQ' + K'Q$$

 (b) Truth table and characteristic equation




(c) J-K flip-flop timing

T FF Timing Diagram



FIGURE 11-27
Timing Diagram for
T Flip-Flop (Falling-
Edge Trigger)

© Cengage Learning 2014

 


(Falling-Edge Triggered)

Additional Inputs

  

Sequential Circuits

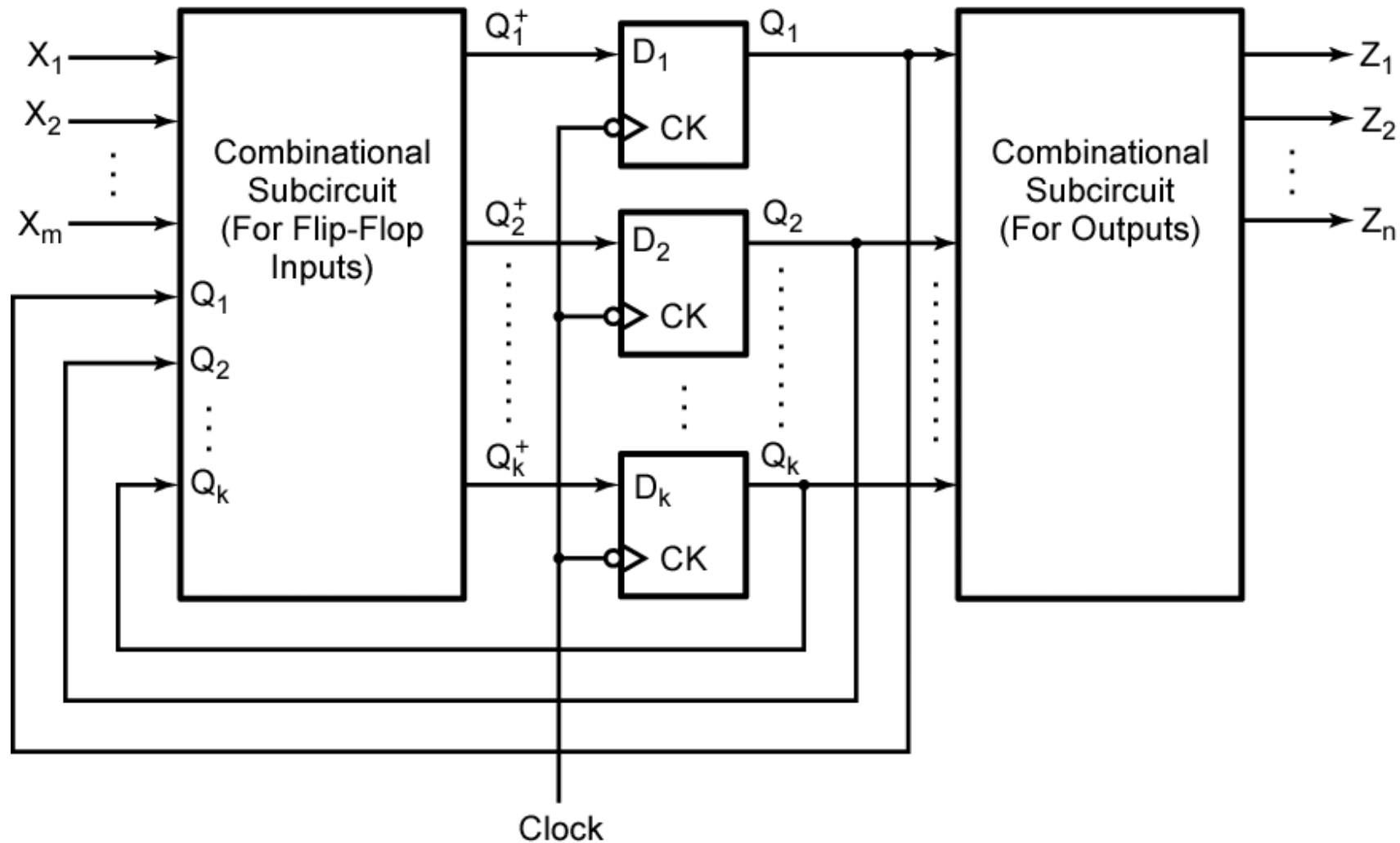

Summary

- ◆ Latches
 - S-R (Set-Reset)
 - D (Data)
- ◆ Flip-Flops (Edge-Triggered)
 - D (Data)
 - J-K (Set-Reset-Toggle)
 - T (Toggle)