

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 3

The Field Effect Transistor

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-1

In this chapter, we will:


- Study and understand the operation and characteristics of the various types of MOSFETs.
- Understand and become familiar with the dc analysis and design techniques of MOSFET circuits.
- Examine three applications of MOSFET circuits.
- Investigate current source biasing of MOSFET circuits, such as those used in integrated circuits.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-2

Basic Structure of MOS Capacitor

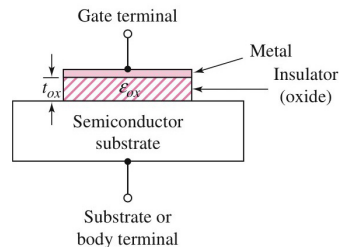

Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-3

MOS Capacitor Under Bias: Electric Field and Charge

Parallel plate capacitor

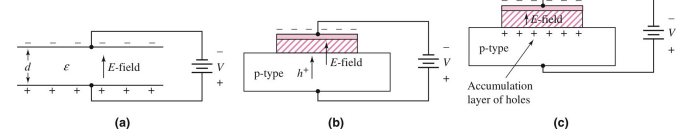

Negative gate bias:

Holes attracted to gate

Positive gate bias:


Electrons attracted to gate

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-4

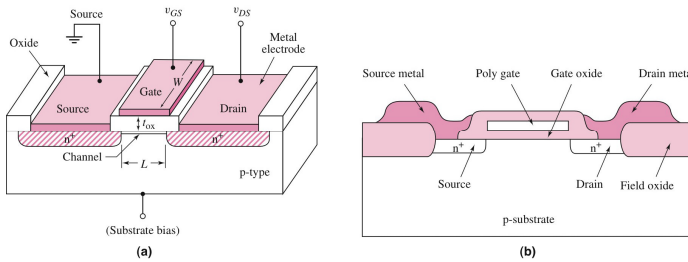Schematic of n-Channel Enhancement Mode MOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-5

Basic Transistor Operation

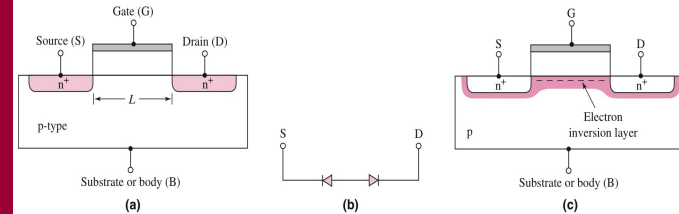
Before electron
inversion layer is
formedAfter electron
inversion layer is
formed

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-6

Basic Transistor Operation

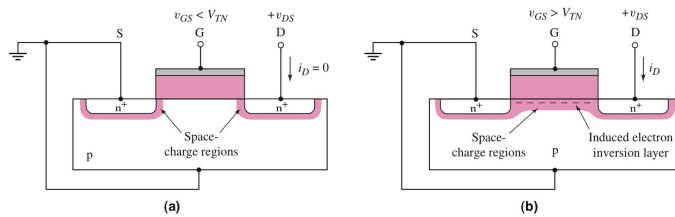


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-7

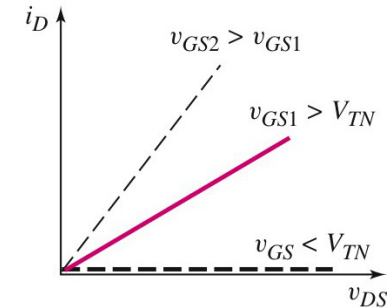Current Versus Voltage Characteristics: Enhancement-Mode nMOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-8

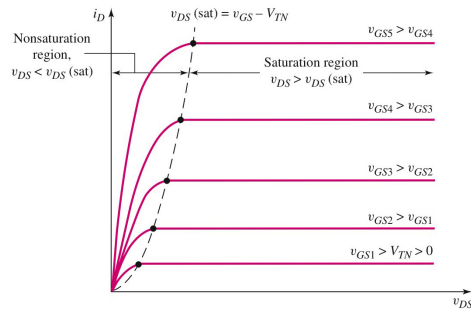Family of i_D Versus v_{DS} Curves: Enhancement-Mode nMOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-9

p-Channel Enhancement-Mode MOSFET

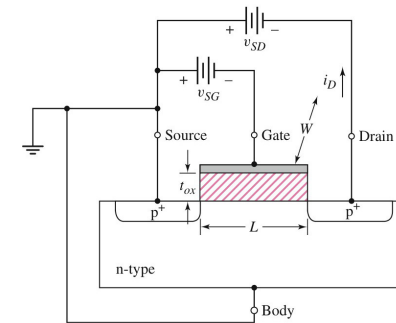


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-10

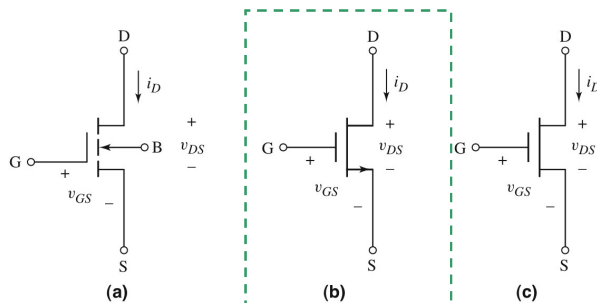Symbols for n-Channel Enhancement-Mode MOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-11

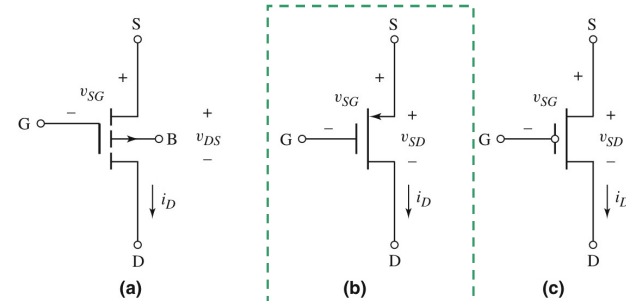Symbols for p-Channel Enhancement-Mode MOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-12

n-Channel Depletion-Mode MOSFET

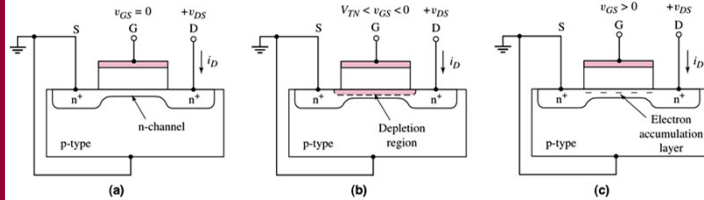


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-13

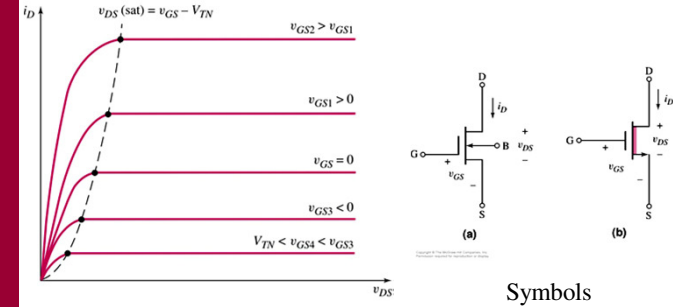Family of i_D Versus v_{DS} Curves: Depletion-Mode nMOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-14

p-Channel Depletion-Mode MOSFET

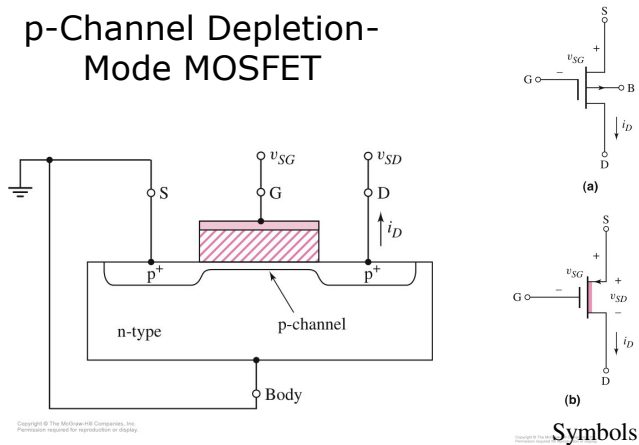


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-15

Cross-Section of nMOSFET and pMOSFET

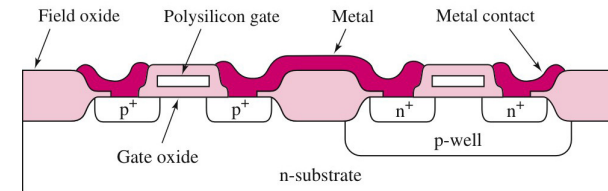Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Both transistors are used in the fabrication of CMOS circuitry.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-16

Summary of I-V Relationships

Region	NMOS	PMOS
Nonsaturation	$v_{DS} < v_{DS}(\text{sat})$ $i_D = K_n [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$	$v_{SD} < v_{SD}(\text{sat})$ $i_D = K_p [2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$
Saturation	$v_{DS} > v_{DS}(\text{sat})$ $i_D = K_n [v_{GS} - V_{TN}]^2$	$v_{SD} > v_{SD}(\text{sat})$ $i_D = K_p [v_{SG} + V_{TP}]^2$
Transition Pt.	$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$
Enhancement Mode	$V_{TN} > 0V$	$V_{TP} < 0V$
Depletion Mode	$V_{TN} < 0V$	$V_{TP} > 0V$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-17

Conduction Parameters

□ NMOSFET

$$K_n = \frac{W\mu_n C_{ox}}{2L} = k'_n \frac{W}{2L}$$

□ PMOSFET

$$K_p = \frac{W\mu_p C_{ox}}{2L} = k'_p \frac{W}{2L}$$

where:


$$C_{ox} = \epsilon_o / t_{ox}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-18

Channel Length Modulation: Early Voltage


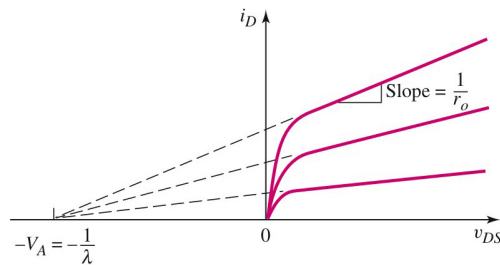
Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-19

Body Effect

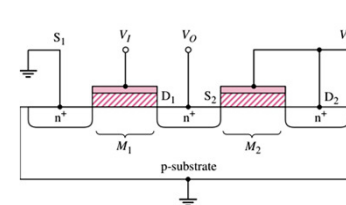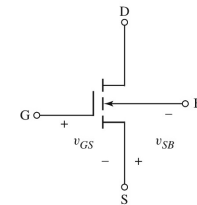
Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-20

Subthreshold Condition

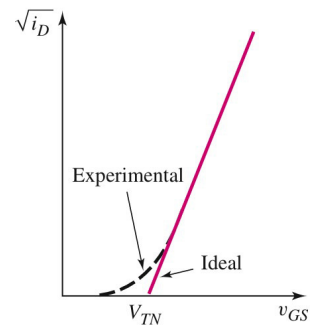




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-21

NMOS Common-Source Circuit

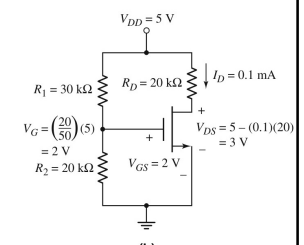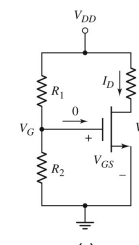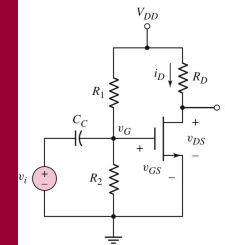




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-22

PMOS Common-Source Circuit

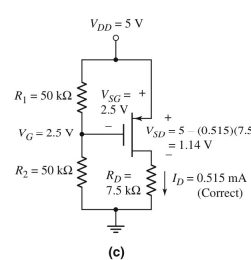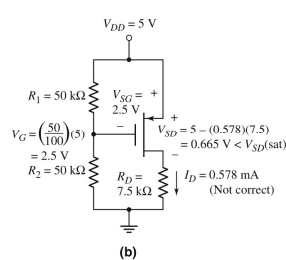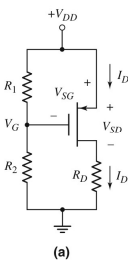


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-23

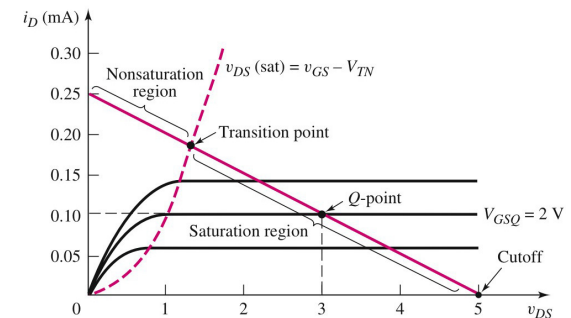Load Line and Modes of Operation: NMOS Common-Source Circuit



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-24

Problem-Solving Technique: NMOSFET DC Analysis


1. Assume the transistor is in saturation.
 - a. $V_{GS} > V_{TN}$, $I_D > 0$, & $V_{DS} \geq V_{DS}(\text{sat})$
2. Analyze circuit using saturation I-V relations.
3. Evaluate resulting bias condition of transistor.
 - a. If $V_{GS} < V_{TN}$, transistor is likely in cutoff
 - b. If $V_{DS} < V_{DS}(\text{sat})$, transistor is likely in nonsaturation region
4. If initial assumption is proven incorrect, make new assumption and repeat Steps 2 and 3.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-25

Enhancement Load Device

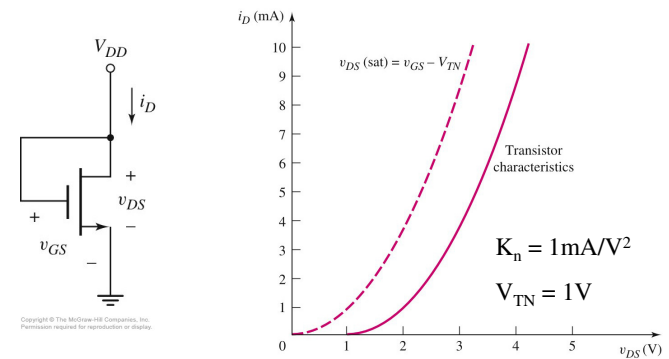


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-26

CMOS Inverter

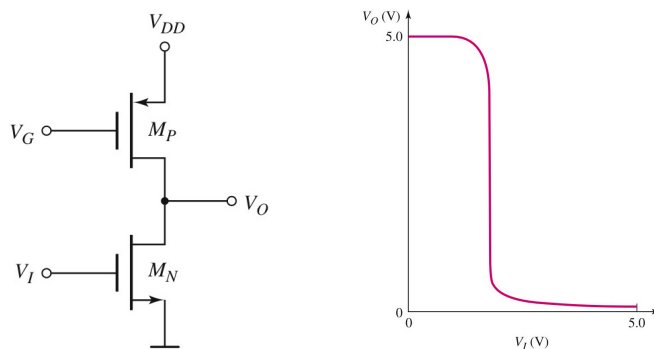


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-27

2-Input NMOS NOR Logic Gate

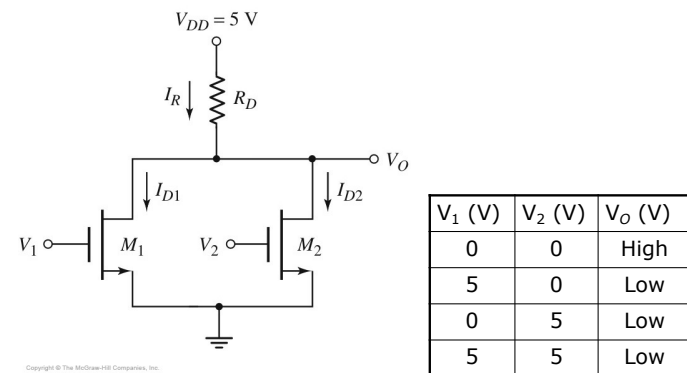


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-28

MOS Small-Signal Amplifier

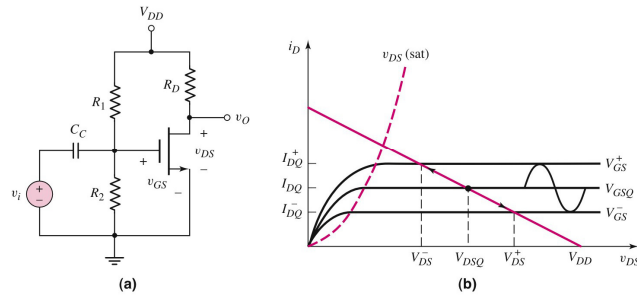


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-29

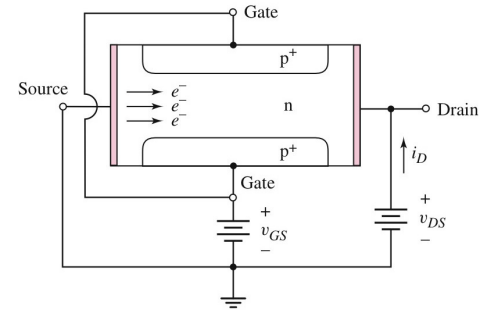Cross Section of n-Channel Junction Field Effect Transistor (JFET)



Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-30