
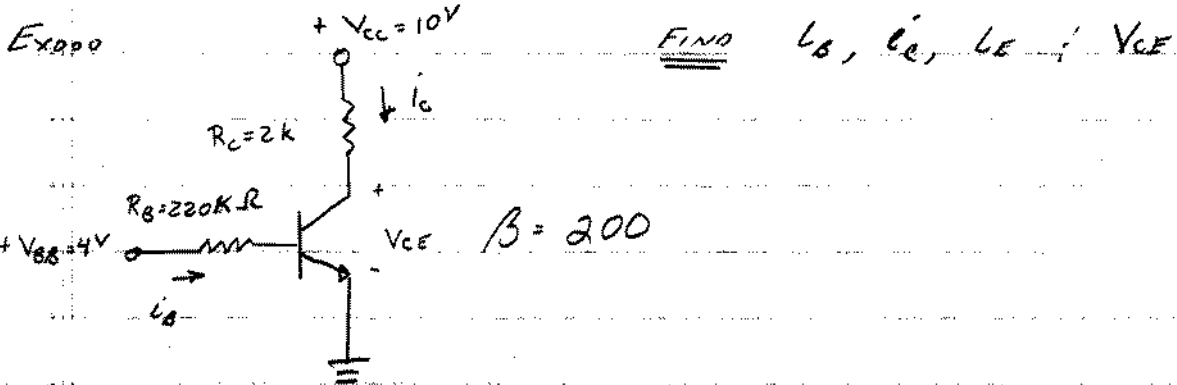


## IV D.C. ANALYSIS : LOAD LINES

### A. THE COMMON EMITTER CIRCUIT

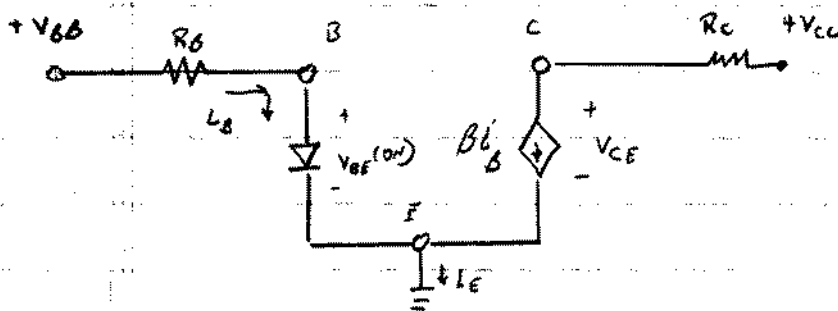

### DC Piecewise Linear Model




- ①  $V_{BE} = 0.7V$
- ②  $I_B = \frac{4 - 0.7}{220k\Omega} = 15\mu A$
- ③  $I_C = \beta I_B = (200)(15\mu A) = 3mA$
- ④  $I_E = (1 + \beta) I_B = 3.02mA$

- ⑤  $V_{CE} = V_{CC} - I_C R_C = 10 - (3)(2) = 4V$

Note: Since  $V_{BB} > V_{BE(on)}$  ;  $V_{CE} > V_{CE(on)} \Rightarrow$  FWO Active Mode

Ex 2.02 PNP Biasing

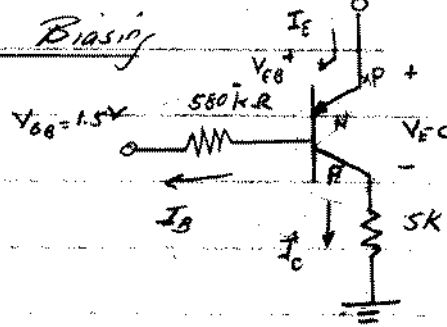Find  $I_B, I_C, I_E, V_{EC}$ 

$$V_{EB} = 0.6$$

$$\beta = 100$$

$$\textcircled{1} \text{ KVL: } +5 + V_{EB} - I_B (580k) + 1.5 = 0$$

$$I_B = \frac{5 - 0.6 - 1.5}{580k} = 5 \mu A$$

$$\textcircled{2} \quad I_C = \beta I_B = 0.5 \text{ mA}$$

$$\textcircled{3} \quad I_E = (\beta + 1) I_B = 0.505 \text{ mA}$$

$$\textcircled{4} \text{ KVL: } -5V + V_{EC} + I_C 5k = 0 \Rightarrow V_{EC} = 5 + (.5)(5) = 2.5V$$


Note: ① The E-B junction is forward biased since  $V_{EC} - V_{EB} > 0.6V$

② The C-B junction is reverse biased since  $V_{EB}(\text{open})$

$$V_{BC} = \underset{\uparrow V_B}{(5 - 0.7)} - \underset{\uparrow V_C}{(-1.5 \times 5)} = 4.3 - 2.5 = 2.8$$

∴ This transistor is in Linear Active mode

$$\text{also: } V_{EC} = 2.5V > V_{EC(ON)} \checkmark$$

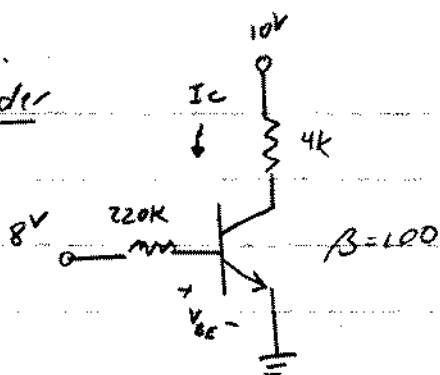Consider

$$\textcircled{1} I_B = \frac{8 - 0.7}{220k} = 33.2 \mu A$$

$$\textcircled{2} I_C = \beta I_B = 3.32 \text{ mA}$$

$$\textcircled{3} V_{CE} = V_{CC} - I_C R_C = 10 - 3.32(4) = -3.28V$$

↑  
CAN'T BE

CAN'T have neg  $V_{CE}$  in Common Emitter NPN. (see characteristic curve)

∴ Transistor is not in Active Region

$$\therefore I_C \neq \beta I_B$$

So: Sat  $V_{CE} = V_{CE}(\text{SAT}) = 0.2V$  ← typical


then:  $I_C = I_C(\text{SAT}) = \frac{V_{CC} - V_{CE}(\text{SAT})}{R_C} = \frac{10 - 0.2}{4k} = 2.45 \text{ mA}$

and  $I_E = I_B + I_C = 33.2 \mu A + 2.45 \text{ mA} = 2.48 \text{ mA}$

Notes: ① Typically  $V_{CE}(\text{SAT}) = \text{constant}$  and is given, this is another piecewise linear approx of the transistor characteristic

②  $I_C/I_B = \frac{2.45}{0.0332} = 74 < \beta$  which is typical of saturation.

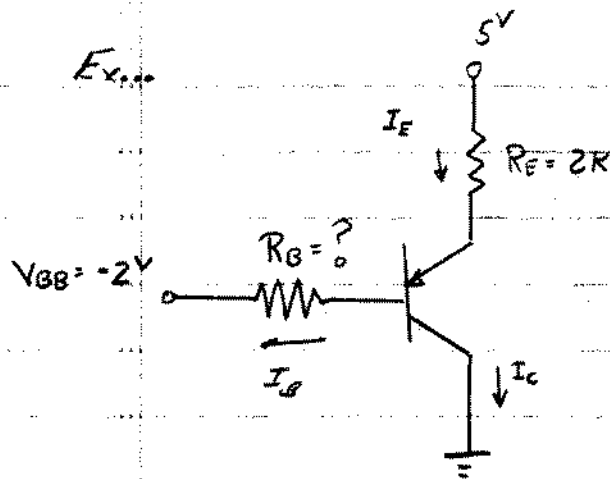So if  $I_C < \beta I_B$  the transistor is in saturation.



Given:  $V_{EB(ON)} = 0.6V$

$\beta = 60$

Find:  $R_B$  so  $V_{ECQ} = 2.5V$

1. EC Loop KVL:  $-5V + I_E 2k + V_{EC} = 0$

$$I_E = \frac{5 - 2.5}{2k} = \underline{1.25 \text{ mA}}$$


2.  $I_C = \frac{\beta}{1+\beta} I_E = \left(\frac{60}{61}\right) 1.25 = \underline{1.23 \text{ mA}}$

3.  $I_B = \frac{I_E}{(1+\beta)} = \underline{0.02 \text{ mA}}$

4. EB Loop KVL:  $-5 + I_E 2k + V_{EB(ON)} + I_B R_B - 2 = 0$

$$R_B = \frac{7 - 0.6 - 1.25(2)}{0.02 \text{ mA}} = \boxed{190k\Omega}$$

Load Line

 


Note: from 1. above

$$V_{EC} = 5V - I_E 2k = 5V - \left(\frac{61}{60}\right) I_C 2k$$

$$V_{EC} = 5 - I_C (2.03k)$$

Ex...

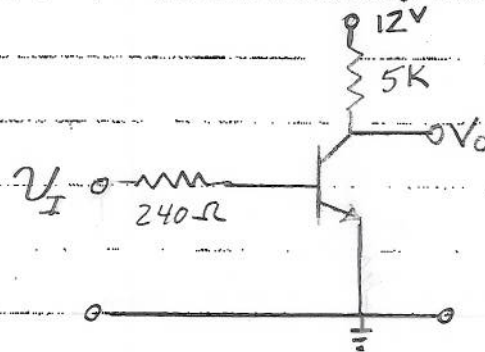Given:  $R_B = 240\Omega$  $V_{CC} = 12V$  $V_{BE(ON)} = 0.7V$  $V_{CE(SAT)} = 0.1$  $\beta = 75$  $R_C = 5\Omega$ Find: currents,  $V_o$ , power dissipated①  $V_i = 0$ : transistor is C-O,  $I_B = I_C = 0$ ,  $V_o = V_{CC} = 12V$ ②  $V_i = 12V$ :  $I_B = \frac{V_i - V_{BE(ON)}}{R_B} = \frac{12 - 0.7}{240} = 47.1 \text{ mA}$ 

Assuming Saturation:

$$I_C = \frac{V_{CC} - V_{CE(SAT)}}{R_C} = \frac{12 - 0.1}{5} = 2.38 \text{ A}$$

$$\text{c.k.: } \frac{I_C}{I_B} \stackrel{?}{<} \beta$$

$$2.38 / 0.0471 = 50.6 < \beta \checkmark$$

↑  
Large for most  
transistors. Would need  
a power transistor

$$V_o = V_{CE(SAT)} = 0.1V$$


③ power dissipated in transistor =  $P = I_C V_{CE} + I_B V_{BE}$ 

$$= (2.38)(0.1) + (0.0471)(0.7)$$

$$= \underline{\underline{0.271W}}$$

## B. Digital Logic

Consider

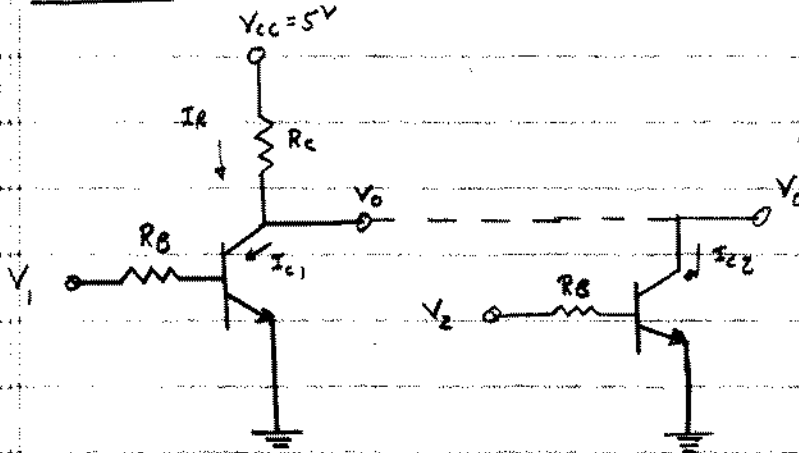

For  $V_1 = 0$ ,  $Q_1$  is cutoff,  $I_B = 0$ ,  $I_C = 0$ ,  $V_0 = V_{CC} = 5V$

For  $V_1 = 5V$ ,  $Q_1$  is SATURATED,  $V_0 = V_{CE} \approx 0.2V$


Now add a second transistor: 2 input NOR GATE

$V_1$	$V_2$	$V_0$
0	0	5V
5	0	0.2V
0	5	0.2
5	5	0.2

Ex 000  $\beta = 50$ ,  $V_{BE(ON)} = 0.7V$ ,  $V_{CE(SAT)} = 0.2V$

$R_E = 1K$ ,  $R_B = 20K$

$V_1$	$V_2$	$V_0$	$I_R$	$Q_1$	$Q_2$
0	0	5	0	$I_{B1} = I_{C1} = 0$	$I_{B2} = I_{C2} = 0$
5	0	0.2	$\frac{5-0.2}{1K} = 4.8mA$	$I_{B1} = \frac{5-0.7}{20K} = 0.215mA$ $I_{C1} = I_R = 4.8mA$	$I_{B2} = I_{C2} = 0$
0	5	0.2	4.8mA	$I_{B1} = I_{C1} = 0$	$I_{B2} = 0.215mA$ $I_{C2} = 4.8mA$
5	5	0.2	4.8mA	$I_{B1} = 0.215mA$ $I_{C1} = I_{C2} = 2.4mA$	$I_{B2} = 0.215mA$ $I_{C2} = \frac{I_R}{2} = 2.4mA$

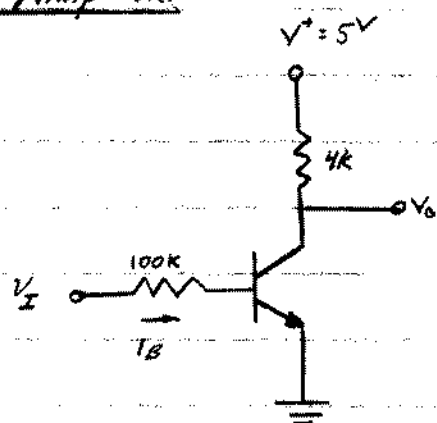
C. Amplifier

$$\beta_F = 100$$

$$V_A = \infty$$

$$V_{BE(on)} = 0.7$$

$$V_{CE(sat)} = 0.2$$

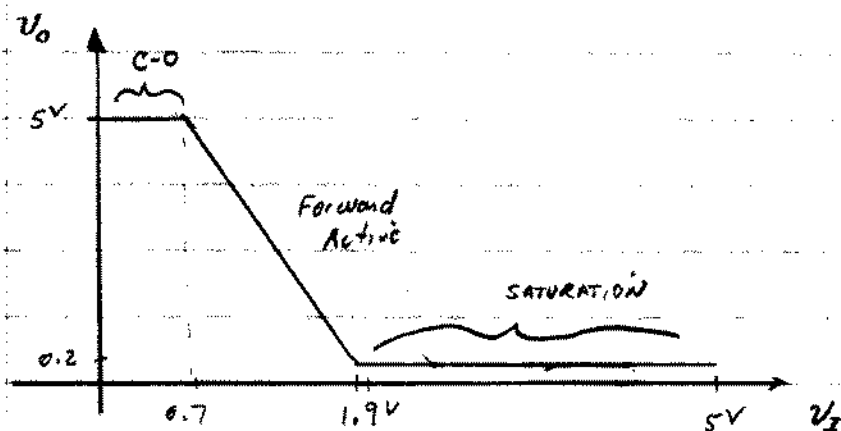SKETCH TRANSFER CHARACTERISTIC ( $V_O$  vs.  $V_I$ )

For  $V_I < 0.7V$ , Q is C=0 ( $V_O = 5V$ )

For  $V_I > 0.7$ , Q is ON  $I_B = \frac{V_I - V_{BE(on)}}{R_E} = \frac{V_I - 0.7}{100k}$


$$V_O = V^+ - \beta I_B R_C = 5 - 100 \left[ \frac{V_I - 0.7}{100k} \right] 4k = 7.8 - 4V_I$$

at  $V_I > 1.9$   $V_O = 0.2$  in SAT



AC Analysis

 - Set  $V_I = 1.3V = V_{BB}$  and input an AC source  $\Delta V_I$ .




Note: 
$$I_B = \frac{V_{BB} + \Delta V_I - V_{BE(on)}}{R_B} = \frac{(1.3 - 0.7) + \Delta V_I}{100k\Omega}$$

$$V_O = V^+ - \beta I_B R_C = 5 - (100) \left[ \frac{0.6 + \Delta V_I}{100k} \right] 4k$$

$$\boxed{V_O = 2.6 - 4\Delta V_I}$$


$$\text{Gain} = A_V = \frac{\Delta V_O}{\Delta V_I} = \boxed{-4}$$

Suppose  $V_I = 1.9V$

 

## B. Single Base Resistor Biasing

1.

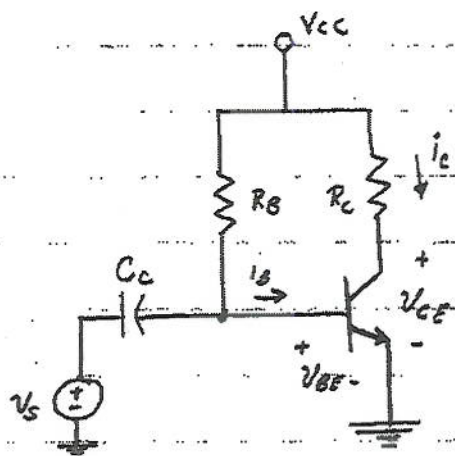

### DC ANALYSIS

#### INPUT CIRCUIT

$$\text{KVL: } I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B}$$

#### OUTPUT CIRCUIT

$$\text{KVL: } I_{CQ} = \frac{V_{CC} - V_{CEQ}}{R_C}$$

Ex. 12. Consider  $V_{CC} = 12\text{V}$ ,  $V_{BE(on)} = 0.7\text{V}$ ,  $R_C = 6\text{k}\Omega$ ,  $R_B = 1.13\text{M}\Omega$ .

then for  $\beta_F = 100$ :

$$I_{BQ} = \frac{V_{CC} - V_{BE(on)}}{R_B} = \frac{12 - 0.7}{1.13\text{M}} = 10\mu\text{A}$$


$$V_{CEQ} = V_{CC} - \beta_F I_B R_C = 12 - (100)(10\mu\text{A})(6\text{k}) = \underline{6\text{V}}$$

for  $\beta_F = 50$ :


$$V_{CEQ} = 12 - (50)(10\mu\text{A})(6\text{k}) = \underline{9\text{V}}$$

50%  $\downarrow \beta_F$ , 50%  $\uparrow V_{CEQ}$
 
# C. Voltage Divider Biasing & the Emitter Resistor



## ANALYSIS

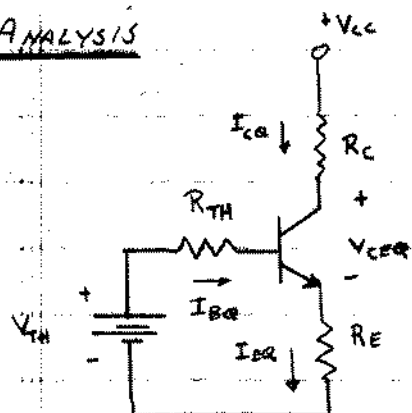

WHERE:  $V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$

$$R_{TH} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Again:  $V_{CEQ} = V_{CC} - \beta_F I_{BQ} R_C$

Hence: KVL:  $-V_{TH} + I_{BQ} R_{TH} + V_{BE} + (\beta_F + 1) I_{BQ} R_E$

So 
$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta_F + 1) R_E}$$

a.o 
$$V_{CEQ} = V_{CC} - \beta_F \left[ \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta_F + 1) R_E} \right] R_C$$


If by design  $R_{TH} \ll (\beta_F + 1) R_E$ ;

then 
$$V_{CEQ} \approx V_{CC} - \left( \frac{\beta_F}{\beta_F + 1} \right) \left[ \frac{V_{TH} - V_{BE}}{R_E} \right] R_C$$

NEARLY  
INDEPENDENT  
OF  $\beta$   
CHANGES.

## D. Integrated Circuit Biasing

Consider :

 

$R_1 - Q_1$  Loop

$$0 = I_1 R_1 + V_{BE(ON)} + V^-$$

$$I_1 = \frac{-(V^- + V_{BE(ON)})}{R_1}$$

ALSO

$$I_1 = I_{C1} + I_{B1} + I_{B2}$$

Assuming  $Q_1, Q_2$  are identical:

$$I_1 = I_{C1} + 2I_{B2} = I_{C2} \left(1 + \frac{2}{\beta}\right)$$

$$I_{C2} = I_Q = \frac{I_1}{1 + \frac{2}{\beta}}$$

Ex. Let  $R_1 = 10k\Omega$ ,  $\beta = 50$ ,  $V_{BE(ON)} = 0.7V$

Then

$$I_1 = \frac{-(V^- + V_{BE(ON)})}{R_1} = \frac{-(-5 + 0.7)}{10k} = 0.43mA$$

$$I_{C2} = \left(\frac{I_1}{1 + \frac{2}{\beta}}\right) = \frac{0.43mA}{(1 + \frac{2}{50})} = 0.413mA$$

$$I_{B1} = I_{B2} = \frac{I_{C2}}{\beta} = \frac{0.413}{50} = 8.26\mu A$$