

Three Phase Systems

- Generation of Three Phase Voltages
- Three Phase Power
- Three Phase Circuit Analysis

Three Phase Systems

- Nearly all electric power generated and distributed is in the form of 3 phase AC.
- These systems consists of 3 phase generators, transmission lines and loads.
- Advantages over single phase systems
 - More efficient (more power per kg of metal)
 - Instantaneous power is a constant, not pulsing or oscillating

A 3 phase generator consists of 3 single phase generators w/ equal magnitude but different phase angle (0°, -120°, -240 degrees).
Or $0, -\frac{2\pi}{3}, -\frac{4\pi}{3}$ radians


It is as if each generator was started at different time delays $t = \phi/\omega = (0, \frac{2\pi}{3\omega}, \frac{4\pi}{3\omega})$

Each of these generators could be connect to identical loads as in figure (c). Each producing identical phase delayed currents.


$$I_A = \frac{V < 0}{Z < \theta} = I < -\theta$$

$$I_B = \frac{V < -120}{Z < \theta} = I < -120 - \theta$$
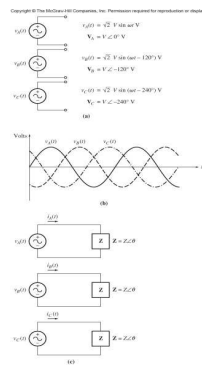
$$I_C = \frac{V < -240}{Z < \theta} = I < -240 - \theta$$



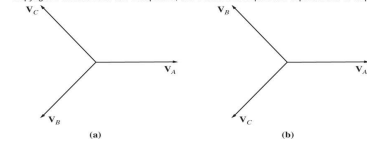Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




a) abc sequence

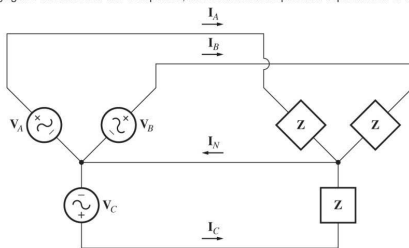b) acb sequence


Can you show that $V_A + V_B + V_C = 0$?

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



We can also connect negative terminals of the three generator and loads together to form a three phase circuit. With the neutral wire only four wires are required. Note: $I_N = I_A + I_B + I_C = 0$ for a balanced 3 phase generator and balanced load.

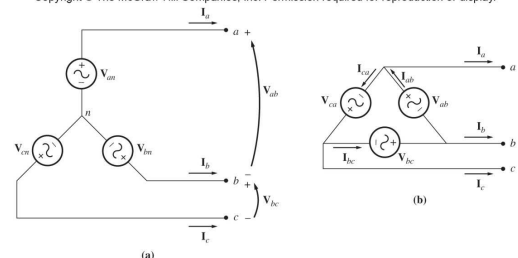Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




a) Y-connected generators

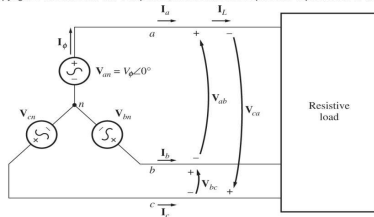b) Δ connected generators

Y connected generator

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Each generator is also called a phase. The voltage and current in a single generator are called the phase voltage (V_ϕ) and phase currents (I_ϕ)

Y connection

- Phase Voltages**

$$\begin{aligned} V_{an} &= V_\phi < 0^\circ \\ V_{bn} &= V_\phi < -120^\circ \\ V_{cn} &= V_\phi < -240^\circ \end{aligned}$$

- Phase Currents (assuming resistive loads)**

$$\begin{aligned} I_a &= I_\phi < 0^\circ \\ I_b &= I_\phi < -120^\circ \\ I_c &= I_\phi < -240^\circ \end{aligned}$$

Y connection

- Line (to Line) Voltages**


$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V_\phi < 0^\circ - V_\phi < -120^\circ \\ &= \sqrt{3}V_\phi < 30^\circ \end{aligned}$$

$$V_{LL} = \sqrt{3}V_\phi \quad Y \text{ connection}$$

- Phase Currents = Line currents**


$$I_a = I_\phi = I_L \quad Y \text{ connection}$$

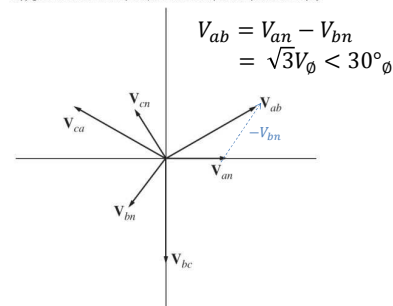Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



DELTA CONNECTED GENERATOR

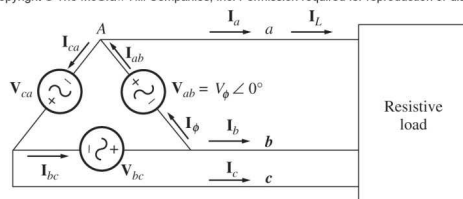Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Δ connection

- Line Voltages = Phase voltages**

$$\begin{aligned} V_{ab} &= V_\phi < 0^\circ \\ V_{bc} &= V_\phi < -120^\circ \\ V_{ca} &= V_\phi < -240^\circ \end{aligned}$$

- Line Currents (assuming resistive loads)**

$$\begin{aligned} I_a &= I_{ab} - I_{ca} = I_\phi < 0^\circ - I_\phi < 120^\circ \\ I_a &= \sqrt{3}I_\phi < -30^\circ \end{aligned}$$


Δ connection

- Line (to Line) Voltages

$$V_{ab} = V_{LL} \quad \Delta \text{ connection}$$

- Phase Currents = Line currents
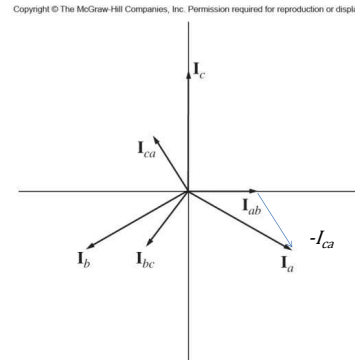
$$I_a = I_L = \sqrt{3} I_\phi \quad \Delta \text{ connection}$$



Three Phase Power


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

$$\begin{aligned}
 v_{an}(t) &= \sqrt{2} V_\phi \cos(\omega t) \\
 v_{bn}(t) &= \sqrt{2} V_\phi \cos(\omega t - 120^\circ) \\
 v_{cn}(t) &= \sqrt{2} V_\phi \cos(\omega t - 240^\circ) \\
 i_a(t) &= \sqrt{2} I_\phi \cos(\omega t - \theta) \\
 i_b(t) &= \sqrt{2} I_\phi \cos(\omega t - \theta - 120^\circ) \\
 i_c(t) &= \sqrt{2} I_\phi \cos(\omega t - \theta - 240^\circ)
 \end{aligned}$$

$$\begin{aligned}
 p_a(t) &= 2V_\phi I_\phi \cos(\omega t) \cos(\omega t - \theta) = V_\phi I_\phi [\cos(\theta) - \cos(2\omega t - \theta)] \\
 p_b(t) &= 2V_\phi I_\phi \cos(\omega t - 120^\circ) \cos(\omega t - \theta - 120^\circ) = V_\phi I_\phi [\cos(\theta) - \cos(2\omega t - \theta - 240^\circ)] \\
 p_c(t) &= 2V_\phi I_\phi \cos(\omega t - 240^\circ) \cos(\omega t - \theta - 240^\circ) = V_\phi I_\phi [\cos(\theta) - \cos(2\omega t - \theta - 480^\circ)]
 \end{aligned}$$

$$\begin{aligned}
 p_{tot}(t) &= p_a(t) + p_b(t) + p_c(t) \\
 &= 3V_\phi I_\phi \cos(\theta) \\
 &= \text{constant}
 \end{aligned}$$

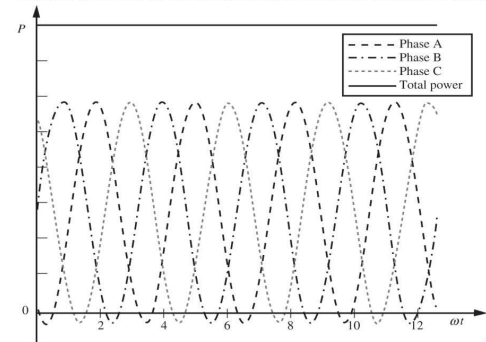Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Power Equations for phase and line quantities

- The power supplied to a balanced three phase load in terms of the phase quantities is:

$$P = 3V_\phi I_\phi \cos(\theta), \quad Q = 3V_\phi I_\phi \sin(\theta), \quad S = 3V_\phi I_\phi$$

- Or equivalently in terms of the line quantities


$$P = \sqrt{3} V_{LL} I_L \cos(\theta), \quad Q = \sqrt{3} V_{LL} I_L \sin(\theta), \quad S = \sqrt{3} V_L I_L$$

Power Equations for phase and line quantities

- All voltages and currents on previous page are RMS values.
- Using the line quantities is generally preferred since easier to measure and equations are same for Y or Δ config.
- Note: θ is angle between phase voltage and phase currents and not between line voltage and line currents.


Analysis of Balanced 3 phase Circuits

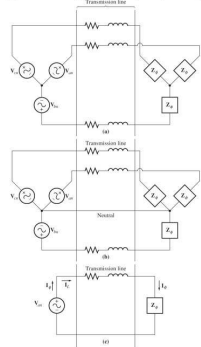Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




- Use a single phase equivalent circuit approach.
- Requires the use of a neutral return path.
- If Δ configuration is encountered it must be converted to a Y

$$Z_Y = \frac{Z_{\Delta}}{3}$$

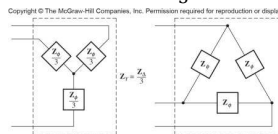


Three Phase Loads

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

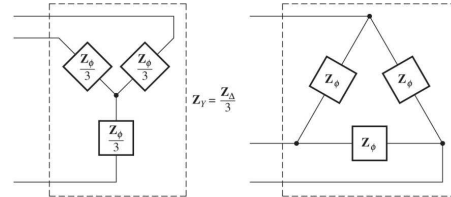

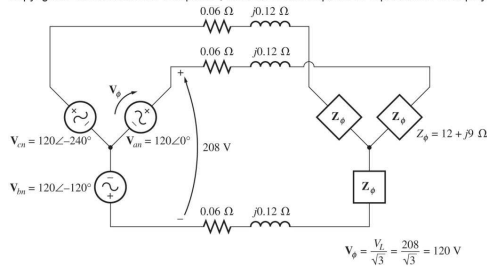
Example 1...

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Solution...

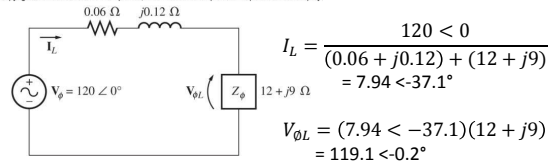Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$P_{Load} = 3V_{\phi}I_{\phi}\cos(\theta) = 3(119.1)(7.94)\cos(36.9) = 2270 \text{ w}$$

$$Q_{Load} = 3V_{\phi}I_{\phi}\sin(\theta) = 3(119.1)(7.94)\sin(36.9) = 1702 \text{ var}$$

$$S_{Load} = 3V_{\phi}I_{\phi} = 3(119.1)(7.94) = 2839 \text{ var}$$

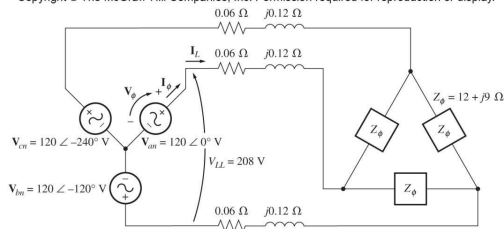
Example 2... Δ connected load

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Solution...

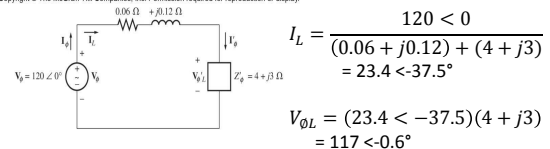Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$P_{Load} = 3V_{\phi}I_{\phi}\cos(\theta) = 3(117)(23.4)\cos(36.9) = 6571 \text{ w}$$

$$Q_{Load} = 3V_{\phi}I_{\phi}\sin(\theta) = 3(117)(23.4)\sin(36.9) = 4928 \text{ var}$$

$$S_{Load} = 3V_{\phi}I_{\phi} = 3(117)(23.4) = 8213 \text{ var}$$


One Line Diagram

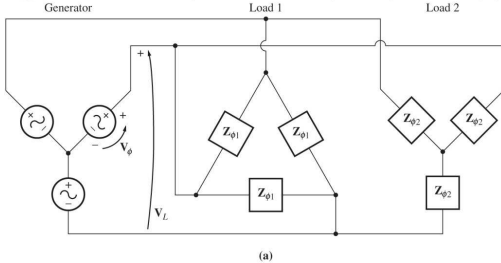Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



One Line Diagram

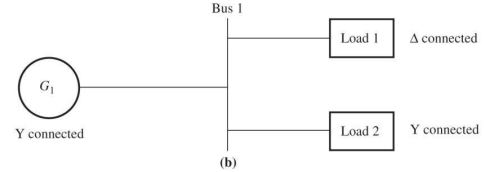
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



If the line transmission lines can be assumed to have negligible impedances, then a one line diagram simplification can be made.

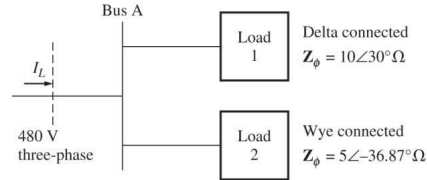Example... Find the total Power.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$I_{\phi 1} = \frac{480}{10} = 48 \text{ A}$$

$$P_1 = 3V_{\phi 1}I_{\phi 1} \cos(30) = 3(480)(48) \cos(30) = 59.9 \text{ kW}$$

$$Q_1 = 3V_{\phi 1}I_{\phi 1} \sin(30) = 3(480)(48) \sin(30) = 34.6 \text{ kVAR}$$

Example continued ... Find the total Power and PF

$$I_{\phi 2} = \frac{480/\sqrt{3}}{5} = 55.4 \text{ A}$$

$$P_2 = 3V_{\phi 2}I_{\phi 2} \cos(-36.87) = 3 \frac{480}{\sqrt{3}} (55.4) \cos(-36.87) = 36.8 \text{ kW}$$

$$Q_2 = 3V_{\phi 2}I_{\phi 2} \sin(-36.87) = 3 \frac{480}{\sqrt{3}} (55.4) \sin(-36.87) = -27.6 \text{ kVAR}$$


$$P_{tot} = 59.9 + 36.8 = 96.7 \text{ kW}$$

$$Q_{tot} = 34.6 + 3 - 27.6 = 7.0 \text{ kVAR}$$

$$\theta = \tan^{-1} \frac{Q}{P} = \tan^{-1} \frac{7}{96.7} = 4.14^\circ$$

$$PF = \cos(\theta) = 0.997 \text{ lagging}$$

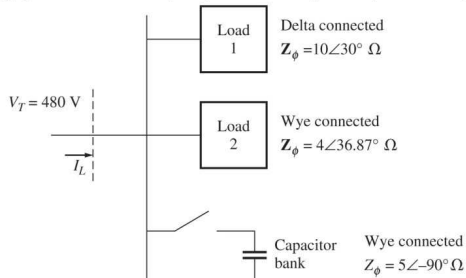Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

