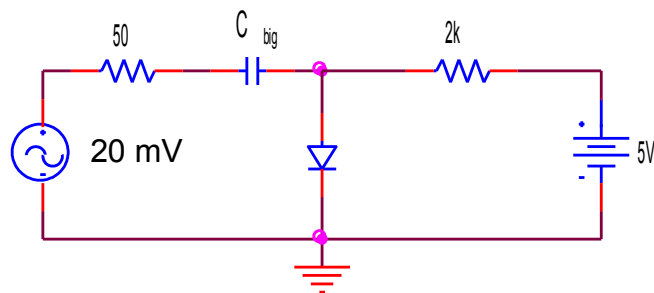






## ELEC 306 Test #1 Sample Problems

- For the circuit shown assume the capacitor is large enough to appear as a short circuit to any AC signals and as an open circuit to any DC signals.



- Using the diode equation, determine  $I_{DQ}$  and  $V_{DQ}$  if  $I_S = 10^{-12} \text{ Amps}$
- Determine the AC voltage across the diode.
- Repeat part a for  $V_g = 0.5 \text{ V}$  and  $r_f = 100 \Omega$

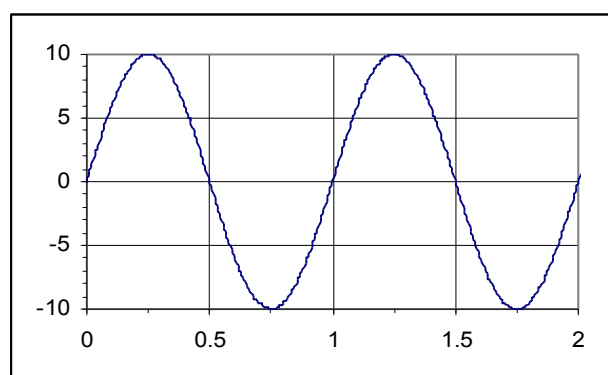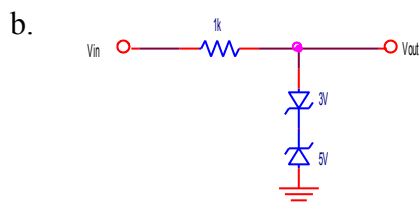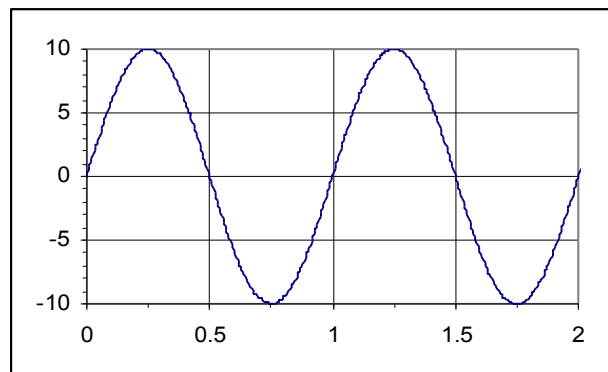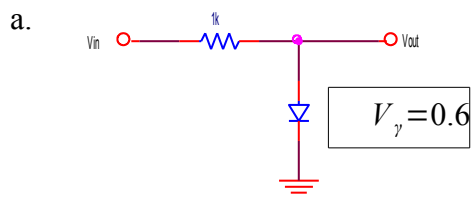- If a  $10V_{pk}$  1kHz sinusoid is applied as  $V_{in}$ , sketch  $V_{out}$  for each of the circuits below



- Design a full wave rectifier circuit to convert 60Hz,  $120V_{RMS}$  AC into  $12V_{DC}$  with  $< 0.5V$  ripple. Assume a load resistance of  $10k\Omega$ .